


IC AUDIO POWER AMPLIFIER



OBJECTIVE:-



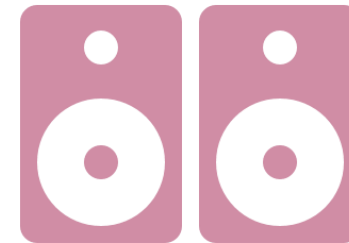(i) To investigate the **gain efficiency** of an IC audio amplifier.



(ii) To investigate the **efficiency** of an IC audio amplifier.

THEORY

1

**(i) Audio
power
Amplifier**

2

(a) Gain of
an Amplifier

3


(b) Efficiency
of Power
Amplifier

4

(c) Bandwidth
of An
Amplifier

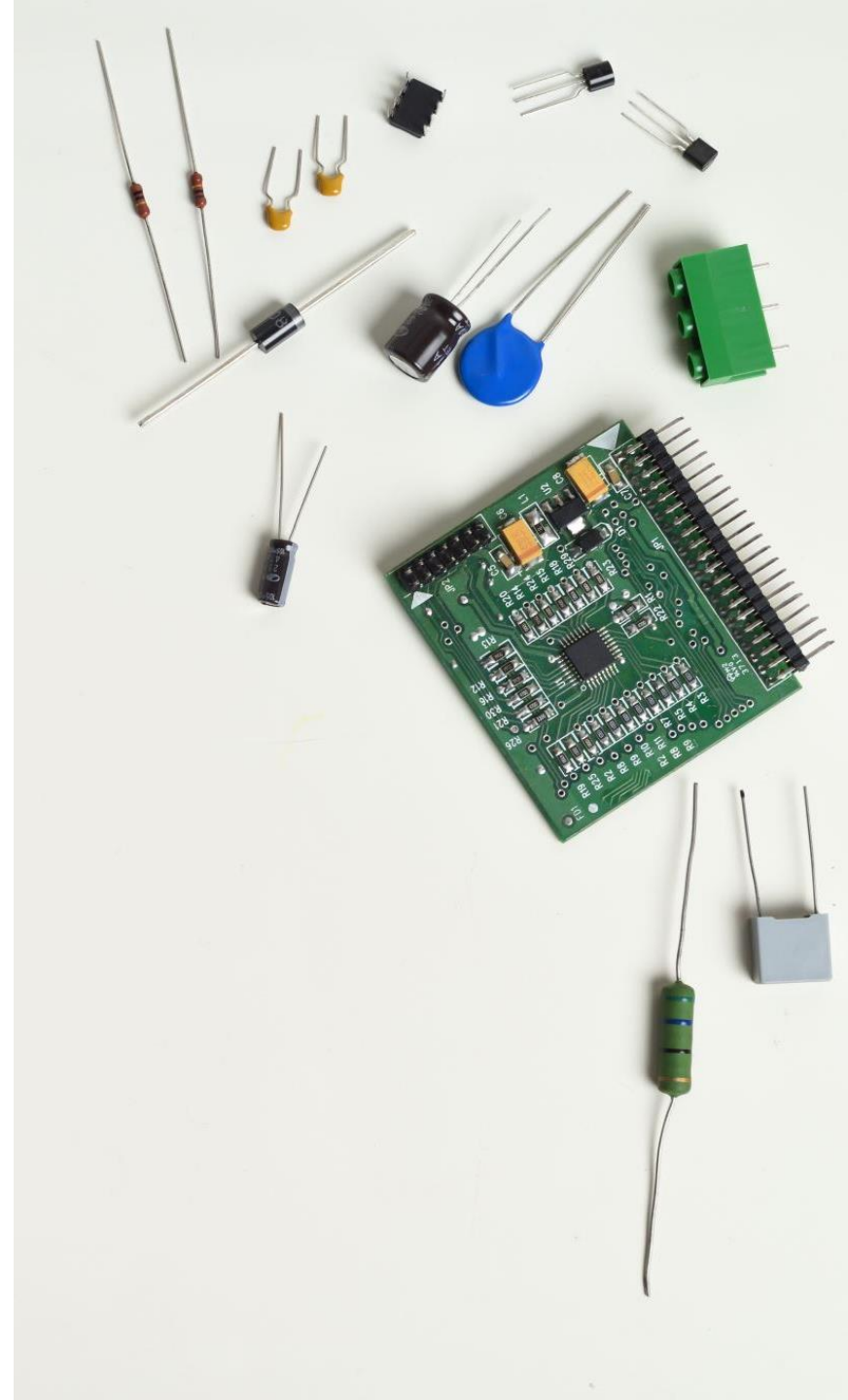
(I) AUDIO POWER AMPLIFIER

- **Equipment and Components Required**
- i. IC audio amplifier -1 pcs
- ii. Signal generator -1 pcs
- iii. Oscilloscope -1 pcs






IC AUDIO AMPLIFIER (SIMULATION)

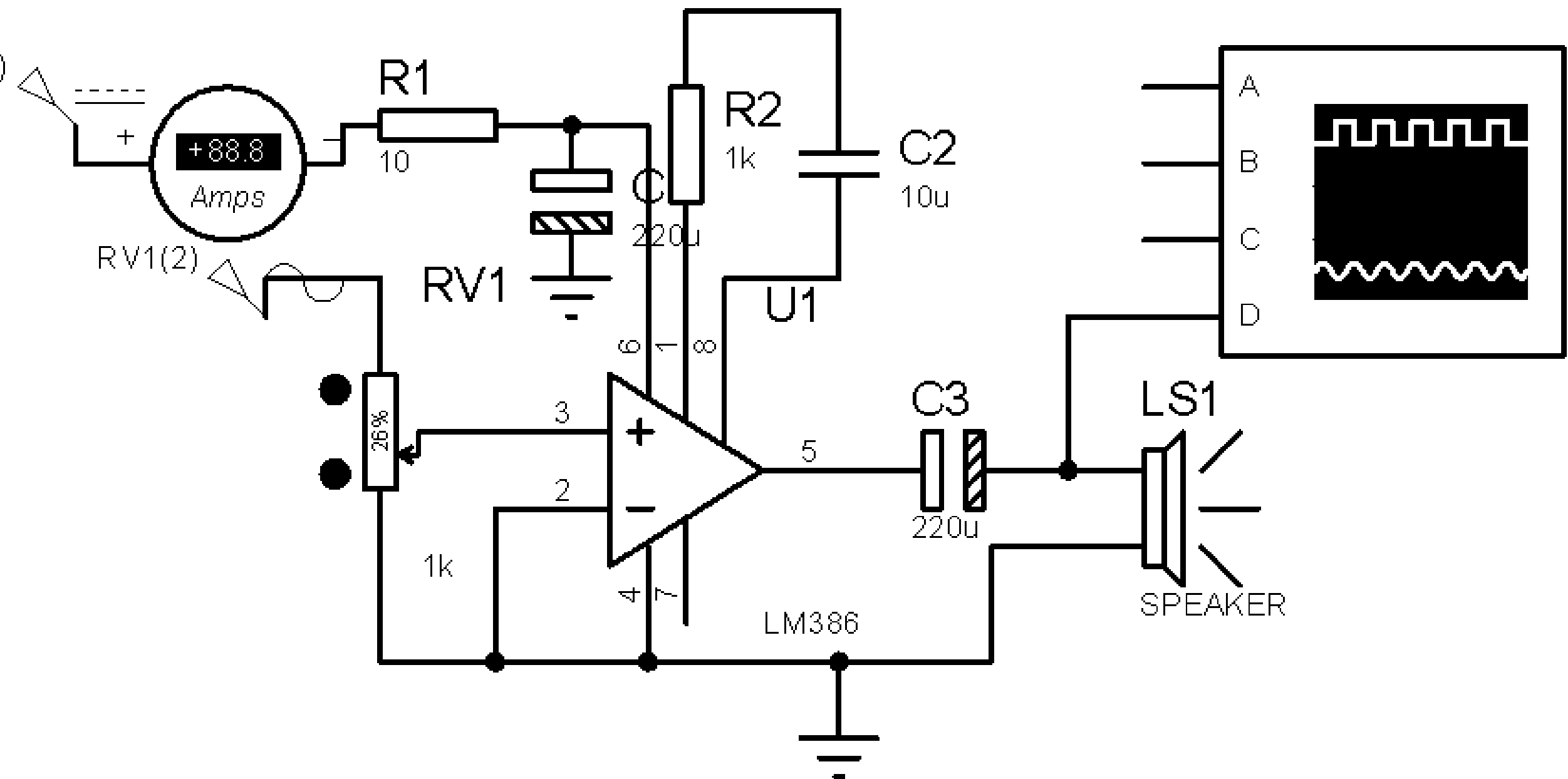

(A) OBSERVATIONS

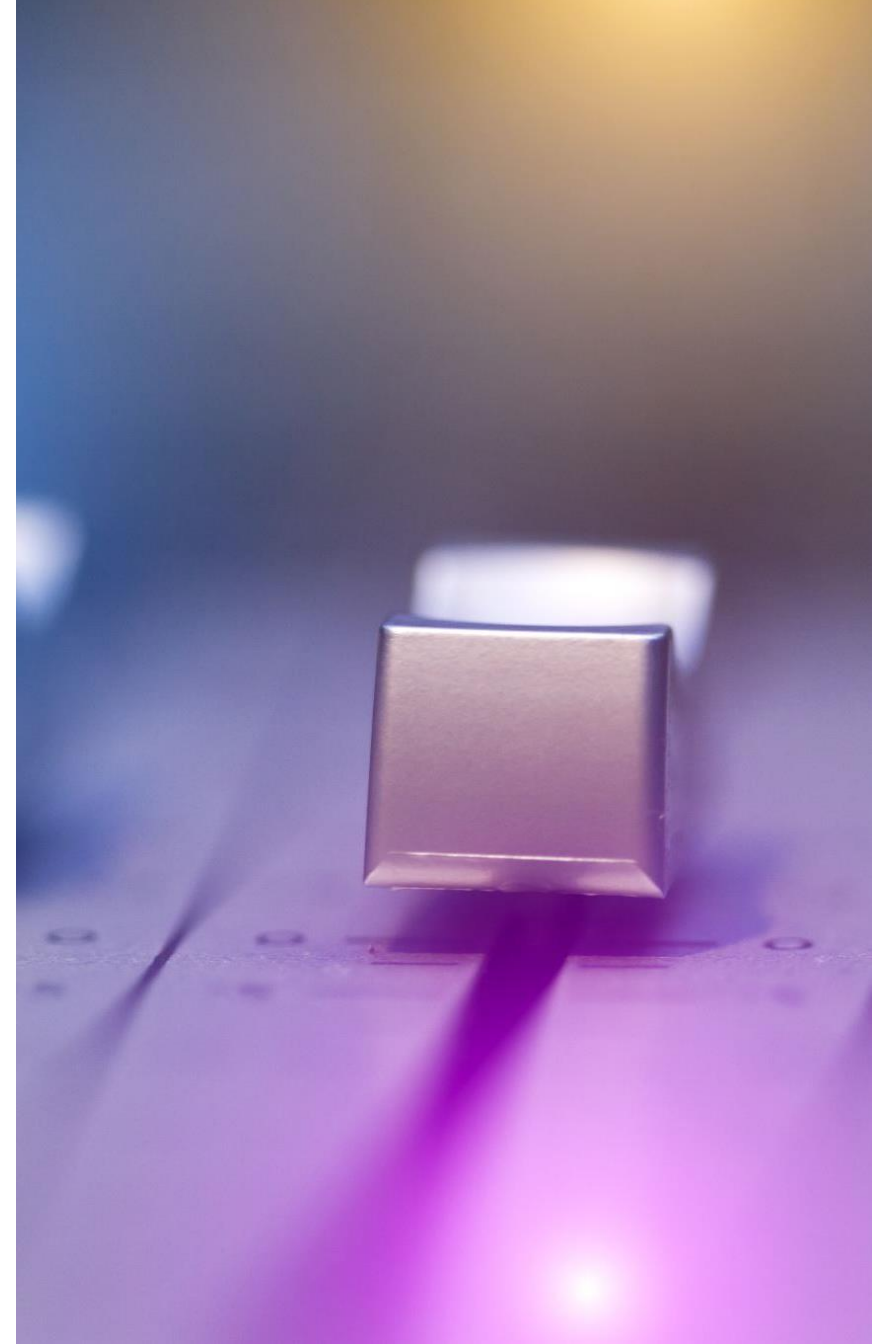- 1. Set the input signal to **100mvp-p (1 KHz)** from the function generator.
- 2. Observe the output of the audio amplifier and calculate the gain and efficiency of the audio amplifier.



CALCULATIONS

$$\text{Gain (A}_v\text{)} = V_{\text{out}} / V_{\text{in}}$$

Output power

$$P_{\text{output}} = (V_{o_{\text{rms}}})^2 / R$$

Where $R=3.2$ (speaker)

$$P_{\text{input}} = V_{\text{in}} * I_{\text{in}}$$

$$\eta = (P_{\text{out}} / P_{\text{in}}) * 100$$

(C) GAIN OF AN AMPLIFIER

V _{opp}	V _{ipp}	A _v

$$\cdot \eta = (P_{out} / P_{in}) * 100$$

AMPLIFIER (B) EFFICIENCY OF POWER