

# Transistor Characteristics

Common Emitter Configuration


# Objectives:-

- To plot and analyze the input characteristics of a common emitter transistor circuit.
- To plot and analyze the output characteristics of a common emitter transistor circuit.


# Theory:-

- Theory should contain
  - (a) Transistor and its types
  - (b) Common Emitter configuration of transistor.
- Input Characteristics of BJT (CE configuration)
  - (a) Relation Between Input voltage  $V_{be}$  and input current  $I_b$  as  $I_b = f(V_{be})$  for  $V_{ce}$  constant.
- Output Characteristics of BJT (CE configuration)
  - (b) Relation Between output voltage  $V_{ce}$  and output current  $I_c$  as  $I_c = f(V_{ce})$  for  $I_b$  Constant.
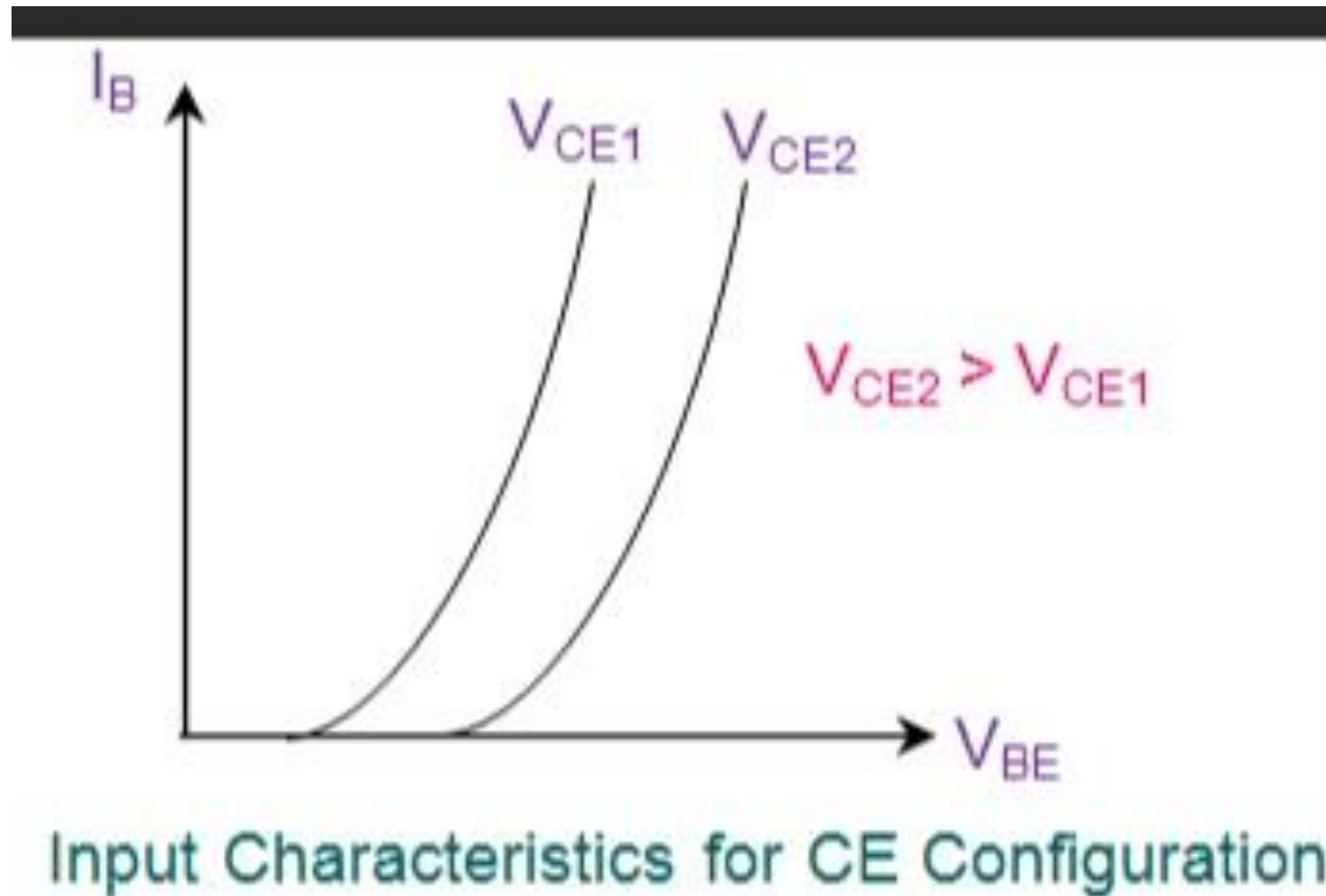
# Transistor I/P characteristic Sample Curve



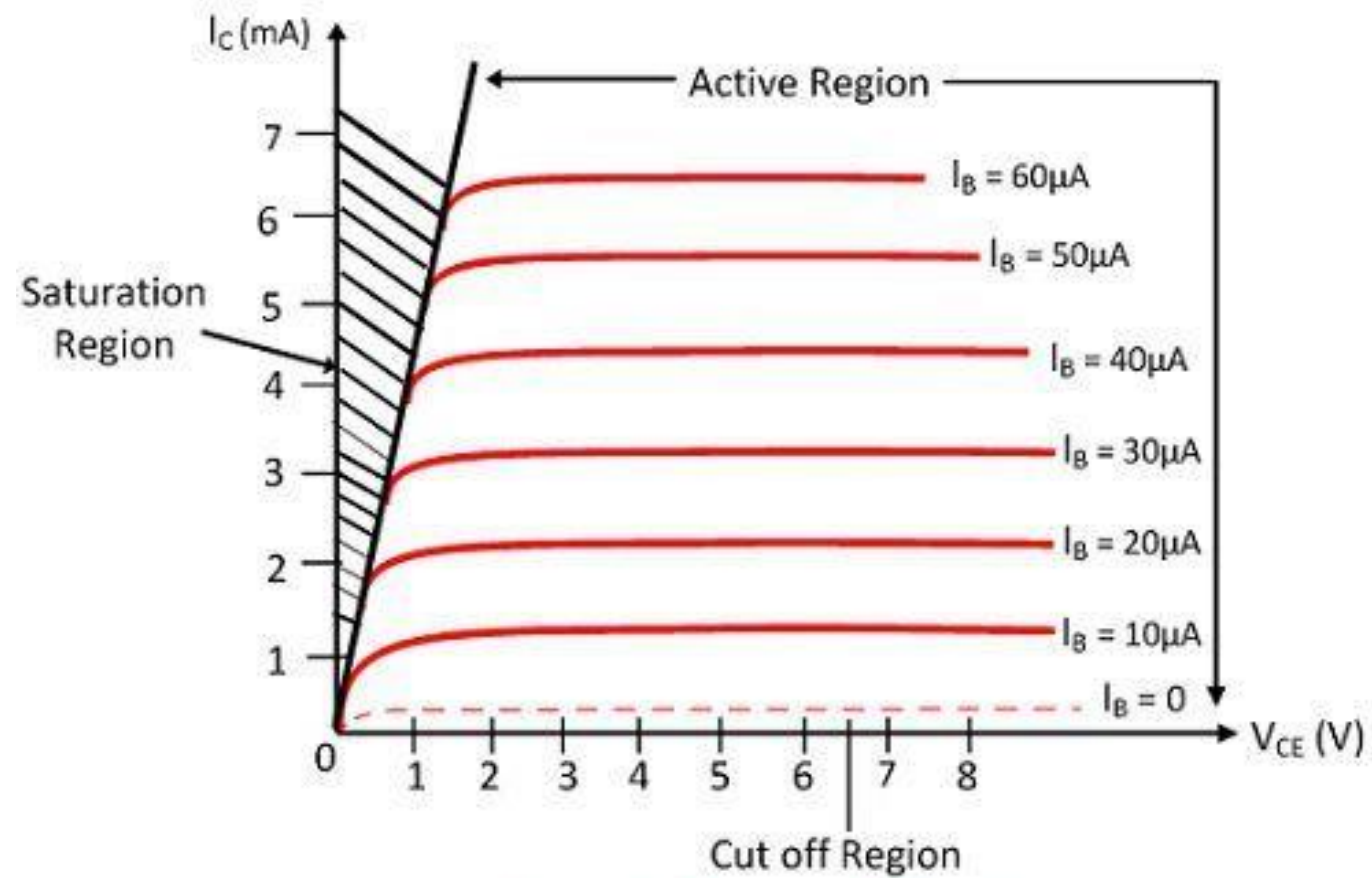
# Transistor o/p characteristic Sample Curve



**Output Characteristic Curve**
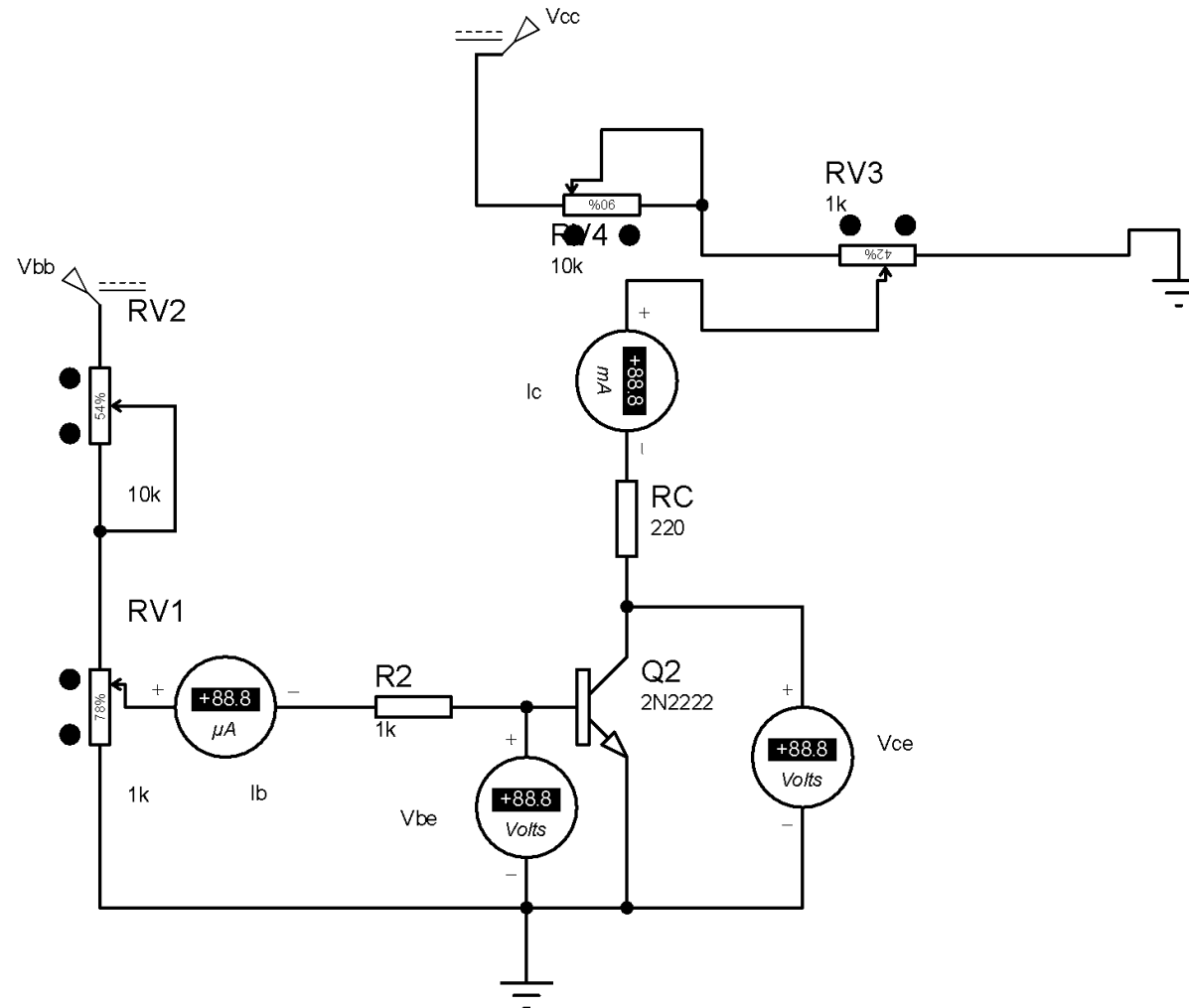
# Transistor Characteristic Circuit Diagram



# Transistor I/P characteristic Table

$V_{be}(v)$	$I_b(ua)$
	0
	0
	5
	10
	20
	50
	100
	150
	200
For $V_{ce}=0$ v constant	

$V_{be}(v)$	$I_b(ua)$
	0
	2
	5
	10
	20
	50
	100
	150
	200
For $V_{ce}= 2$ v constant	

# Transistor O/P characteristic Table

For $I_b = 20\mu\text{A}$ constant	
$V_{ce} \text{ (v)}$	$I_c \text{ (mA)}$
0.1	
0.2	
0.4	
0.8	
1	
2	
3	
4	
5	
8	

For $I_b = 40\mu\text{A}$ constant	
$V_{ce} \text{ (v)}$	$I_c \text{ (mA)}$
0.1	
0.2	
0.4	
0.8	
1	
2	
3	
4	
5	
8	

For $I_b = 80\mu\text{A}$ constant	
$V_{ce} \text{ (v)}$	$I_c \text{ (mA)}$
0.1	
0.2	
0.4	
0.8	
1	
2	
3	
4	
5	
8	



# Sample Graph

